

Birla Institute of Technology Mesra Off Campus Deoghar



EC204 Digital System Design Lab Experiment 1

Name: Harsh Govind
Roll no.: BTECH/60023/20
Semester: III

Date of experiment: 02 Aug 2021


Aim: Verification and interpretation of truth table for AND, OR, NOT, NAND NOR, Ex-OR and Ex-Nor gates.

Apparatus: Logic trainer kit, logic gates / ICs and wires.

Theory: Logic gates are electronic circuits which perform logical functions on one or more inputs to produce one output. There are seven logic gates. When all the input combinations of a logic gate are written in a series and their corresponding outputs written along them, then this input/output combination is called Truth Table.

AND Gate

AND gate produces an output as 1, when all its inputs are 1; otherwise, the output is 0. This gate can have minimum 2 inputs but output is always one. Its output is 0 when any input is 0.

 


IC 7408

A	B	$Y = A.B$
0	0	0
0	1	0
1	0	0
1	1	1


Truth table

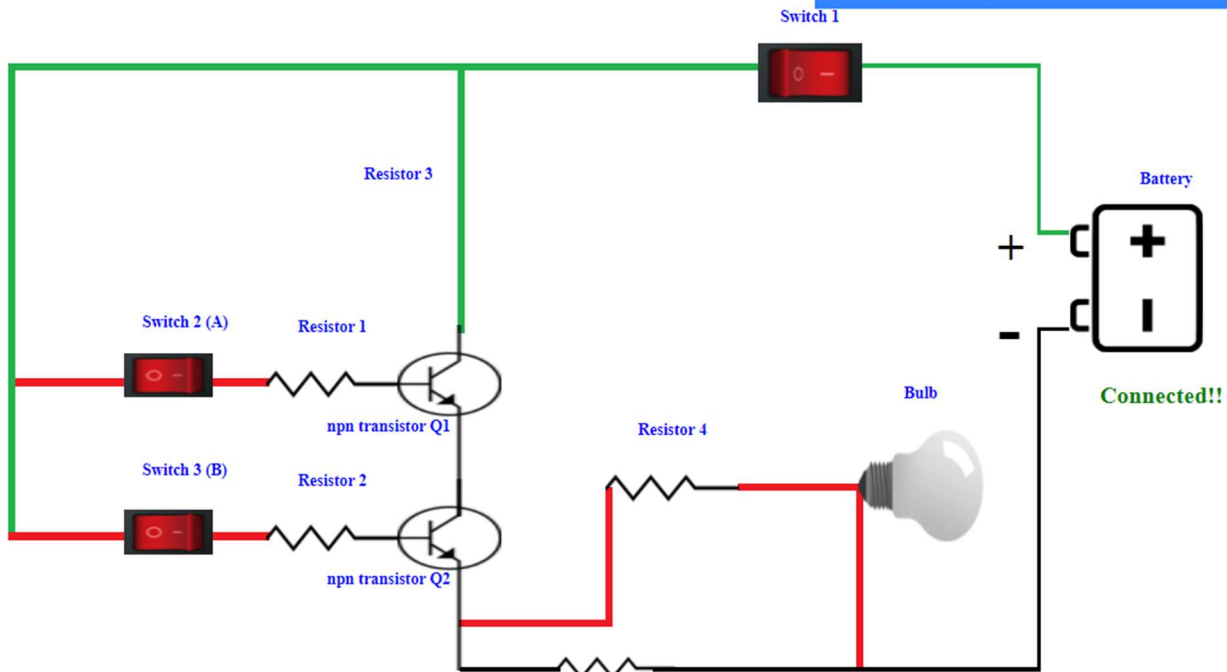AND gate using Resistor-Transistor Logic (RTL)




Both A and B are 0

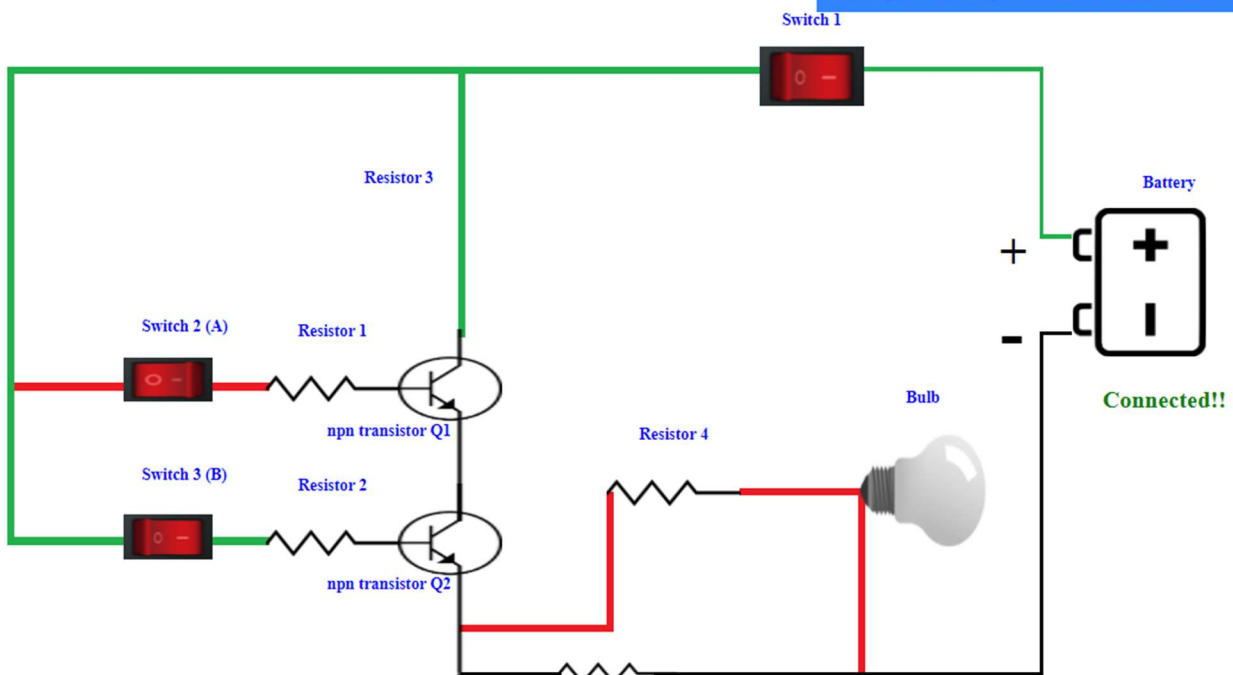AND gate using Resistor-Transistor Logic (RTL)




A = 0 and B = 1

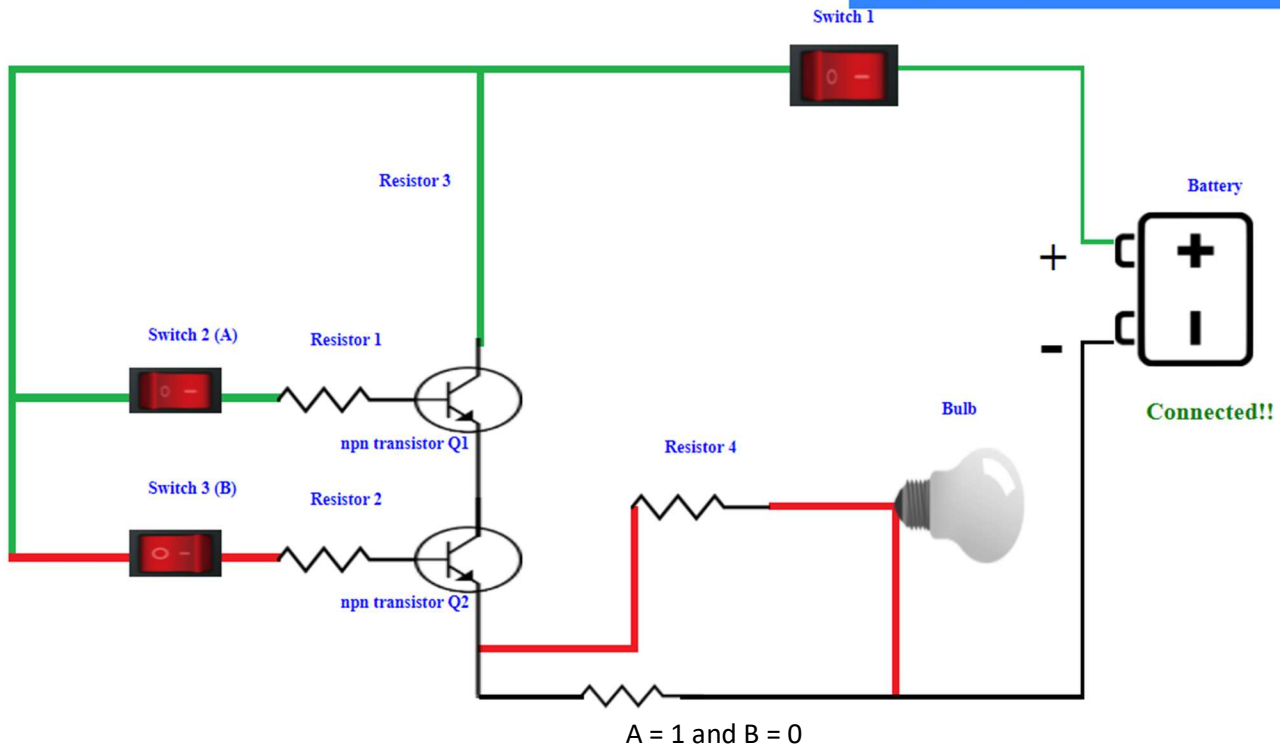AND gate using Resistor-Transistor Logic (RTL)




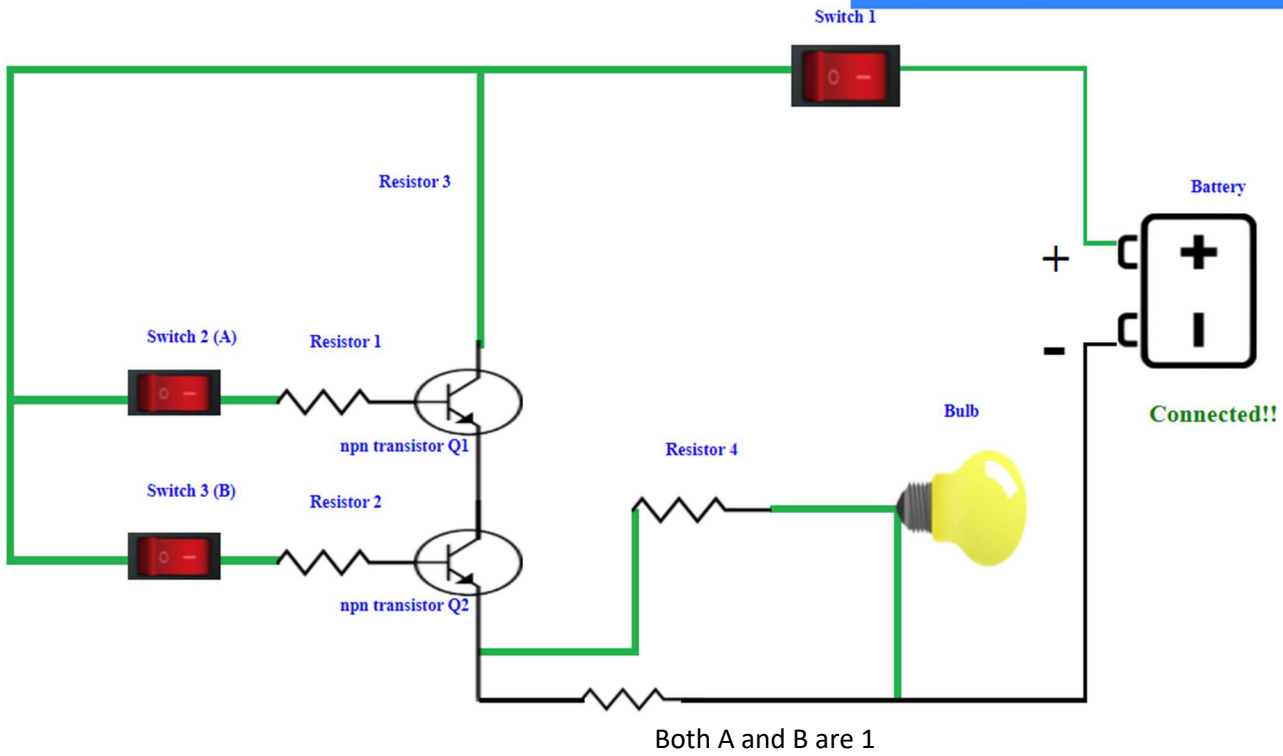AND gate using Resistor-Transistor Logic (RTL)



OR Gate


OR gate produces an output as 1, when any or all its inputs are 1; otherwise the output is 0. This gate can have minimum 2 inputs but output is always one. Its output is 0 when all input are 0.

 


IC 7432

A	B	$Y = A+B$
0	0	0
0	1	1
1	0	1
1	1	1


Truth table

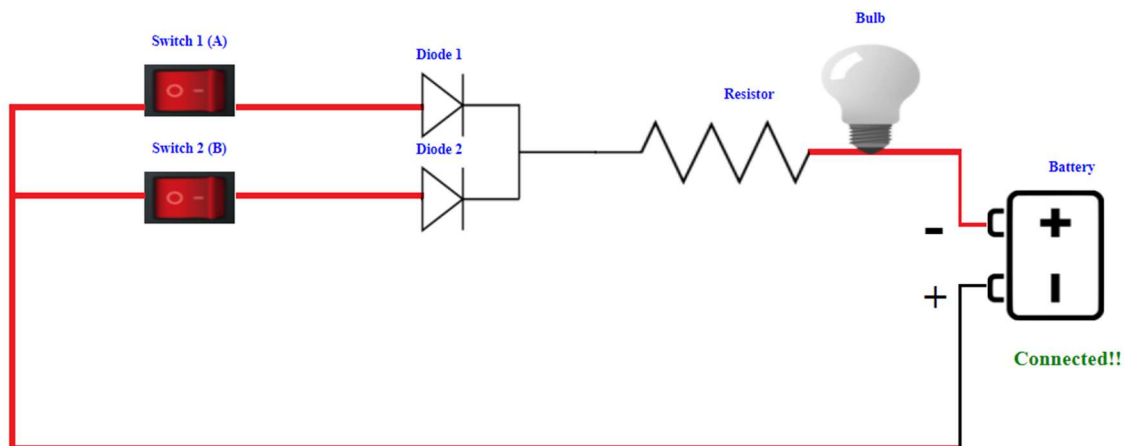


Both A and B are 0

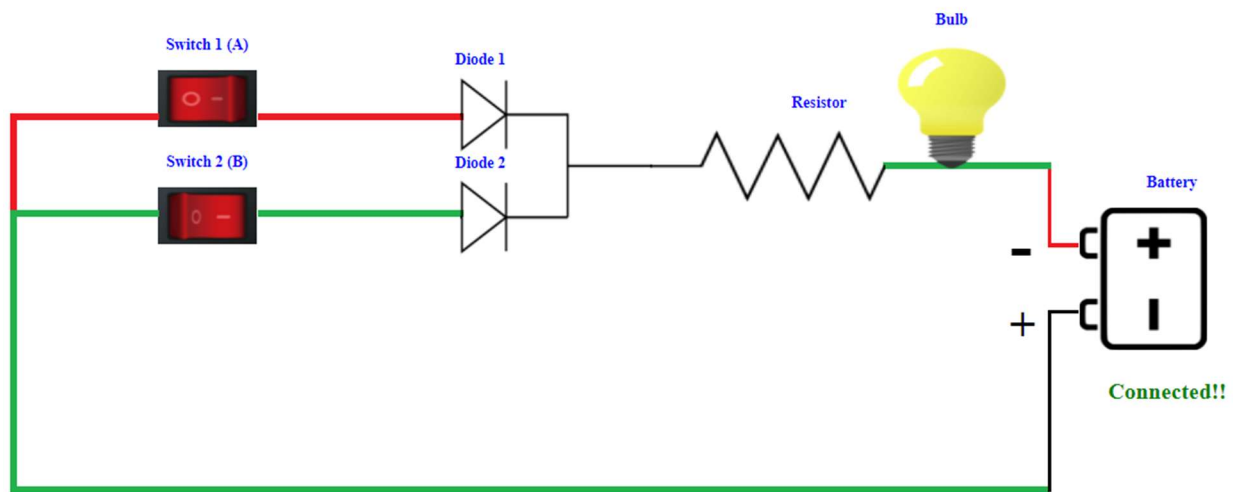

A = 0 and B = 1

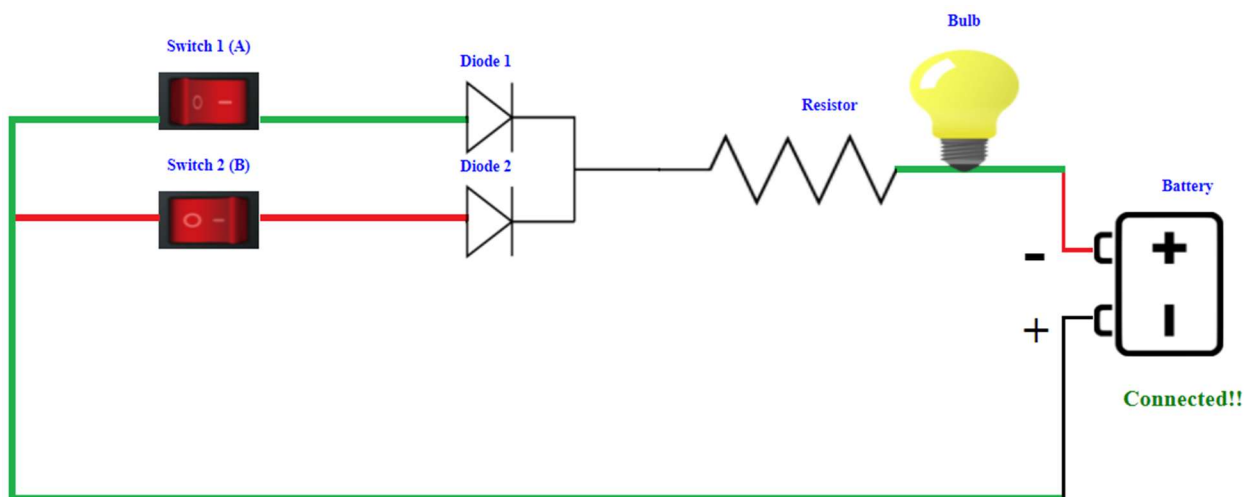


A = 1 and B = 0

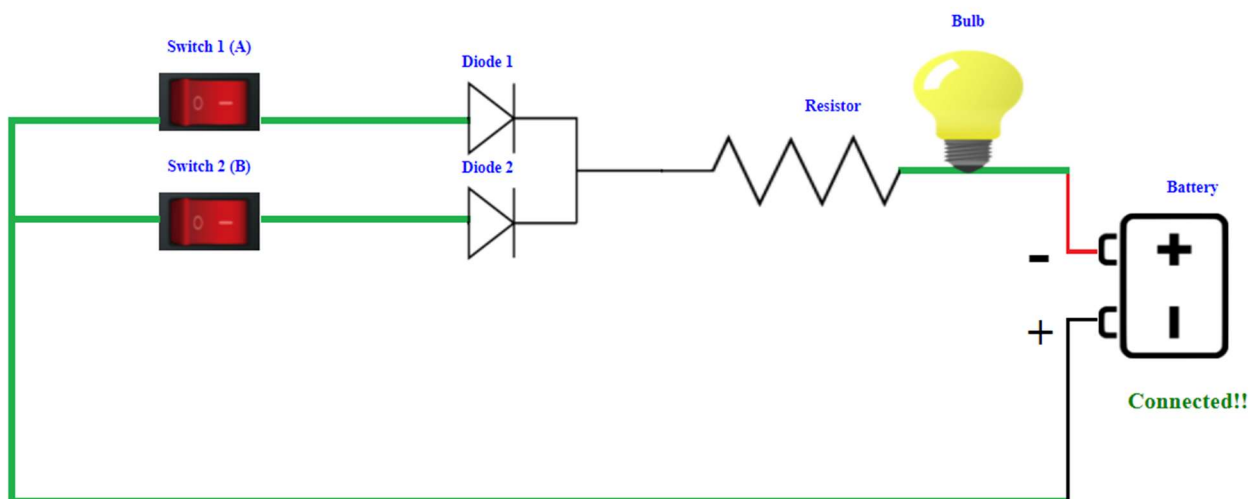

Both A and B are 1

NOT Gate


NOT gate produces the complement of its input. This gate is also called an INVERTER. It always has one input and one output. Its output is 0 when input is 1 and output is 1 when input is 0.

 


IC 7404

A	$Y = A'$
0	1
1	0

Truth table

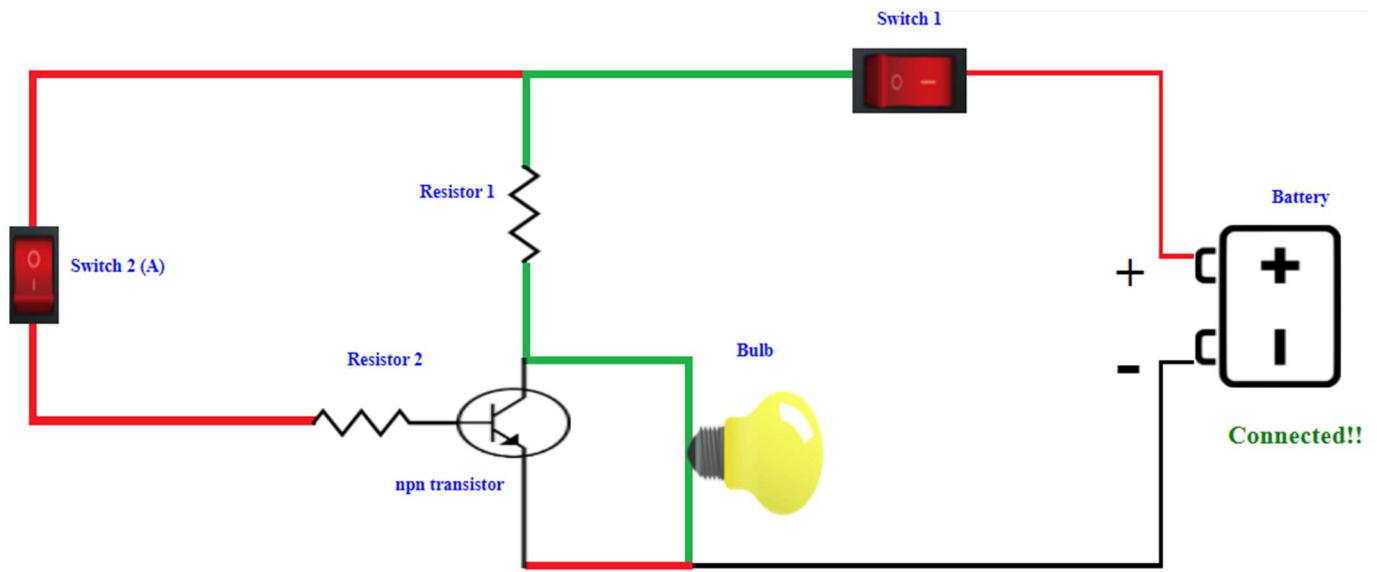


A = 0

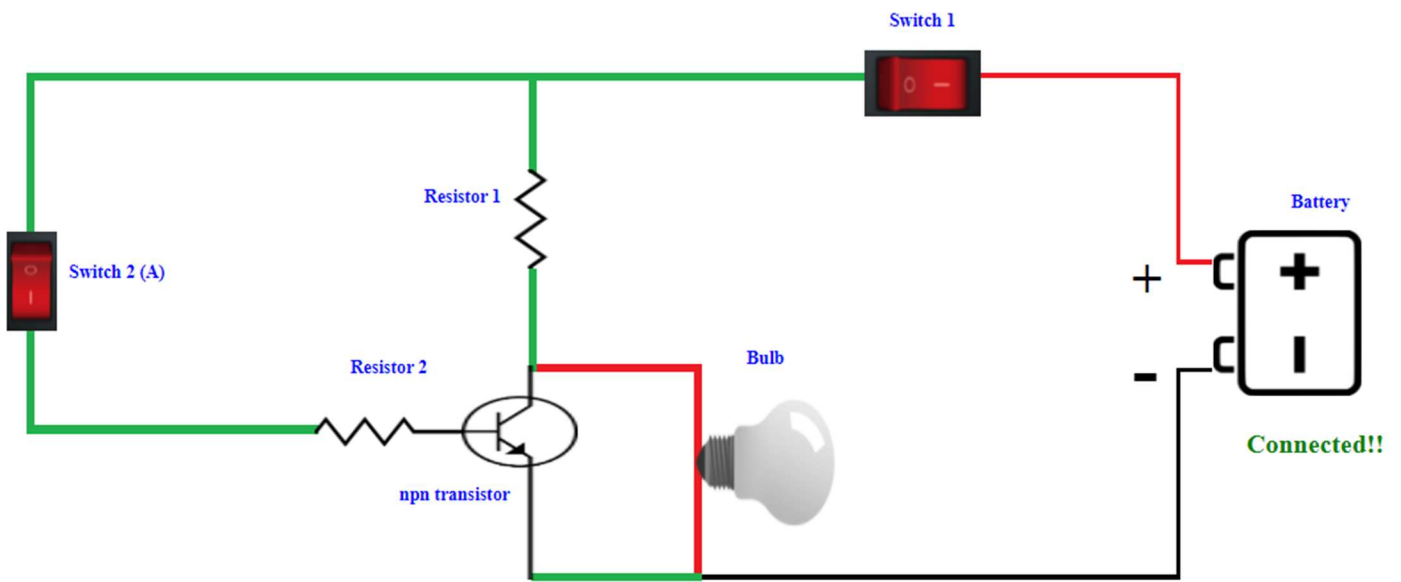

A = 1

NAND Gate



NAND gate is actually a series of AND gate with NOT gate. If we connect the output of an AND gate to the input of a NOT gate, this combination will work as NOT-AND or NAND gate. Its output is 1 when any or all inputs are 0, otherwise output is 1.

 


IC 7400


A	B	$Y = (A.B)'$
0	0	1
0	1	1
1	0	1
1	1	0

Truth table

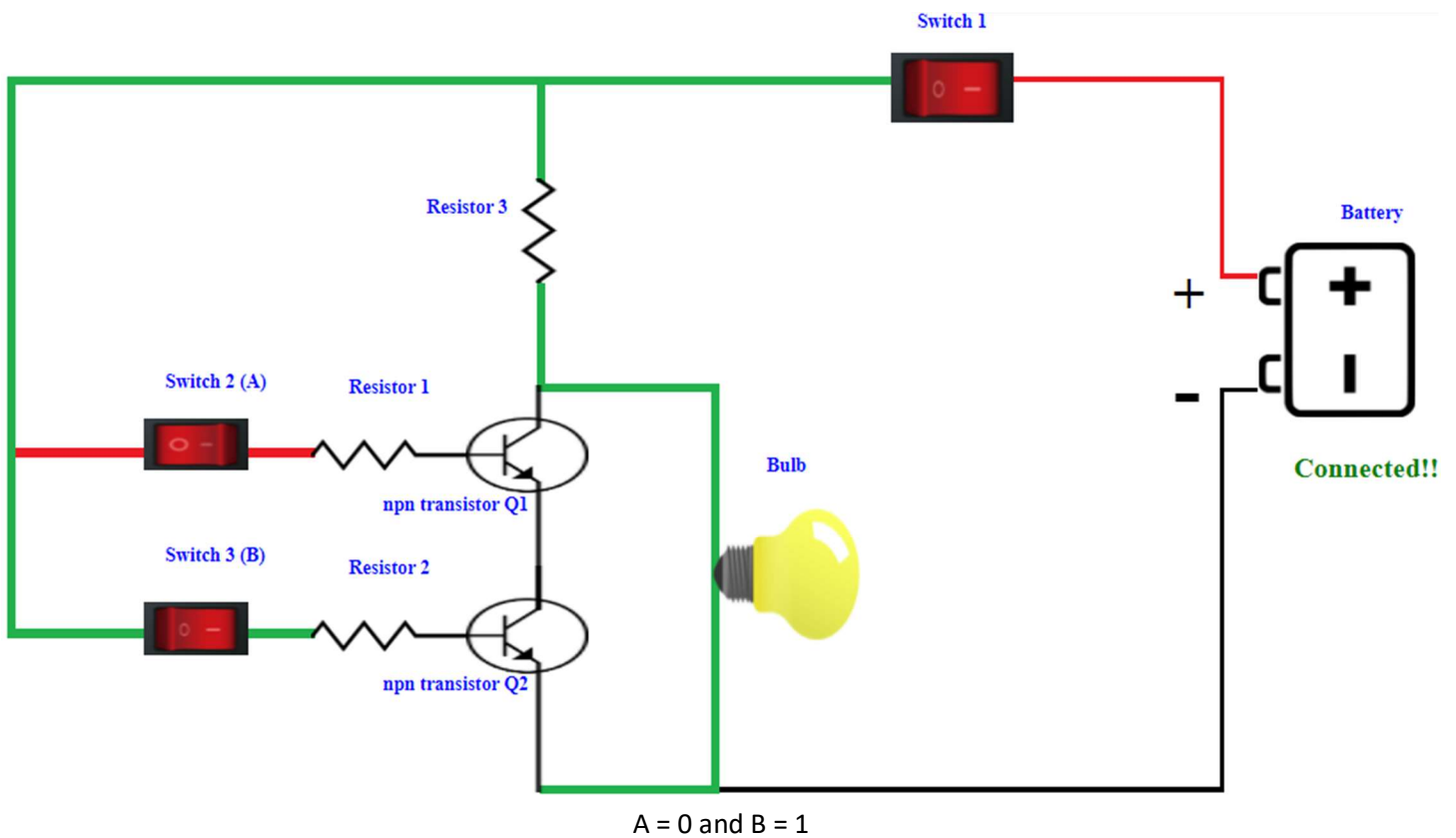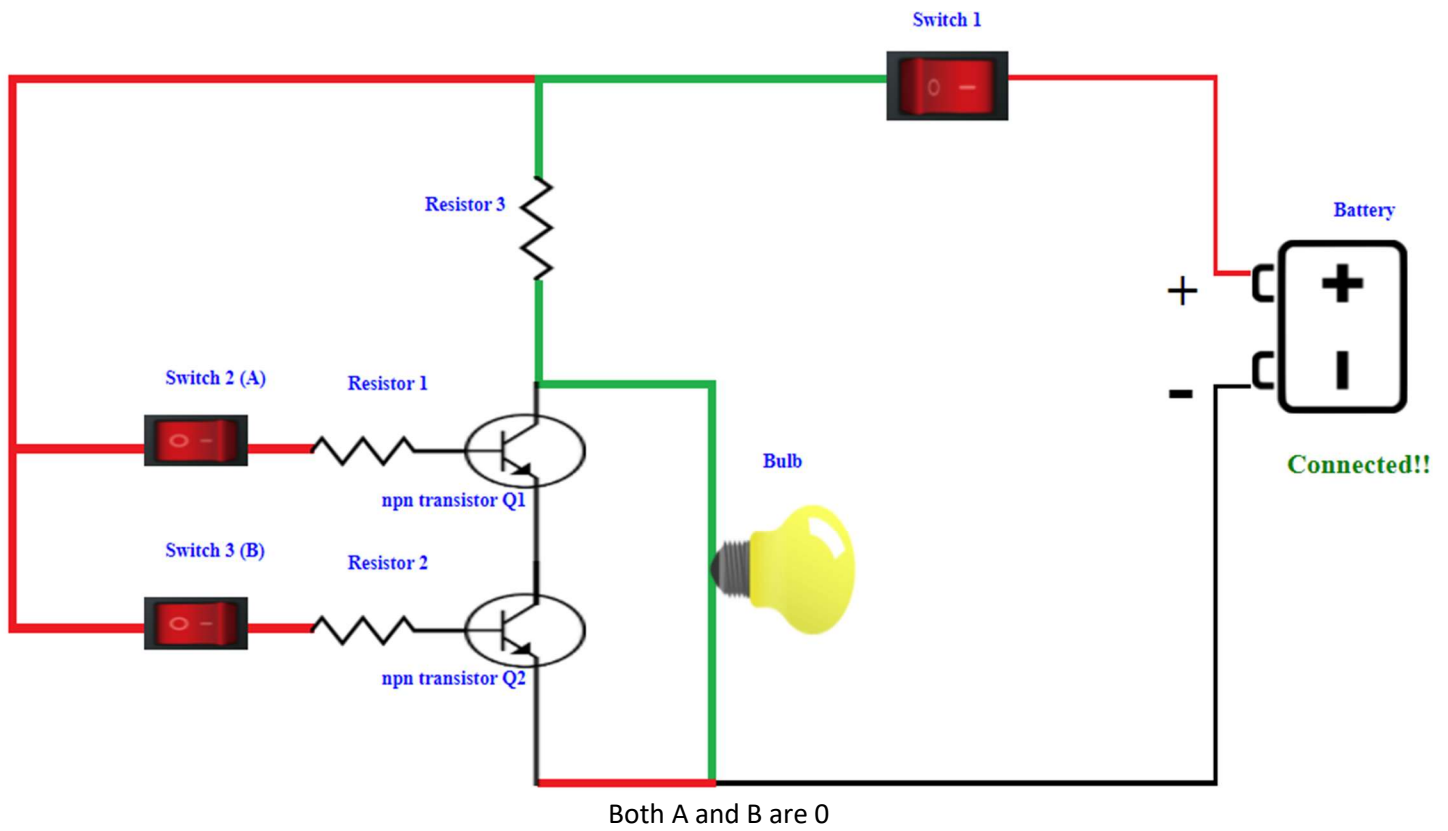

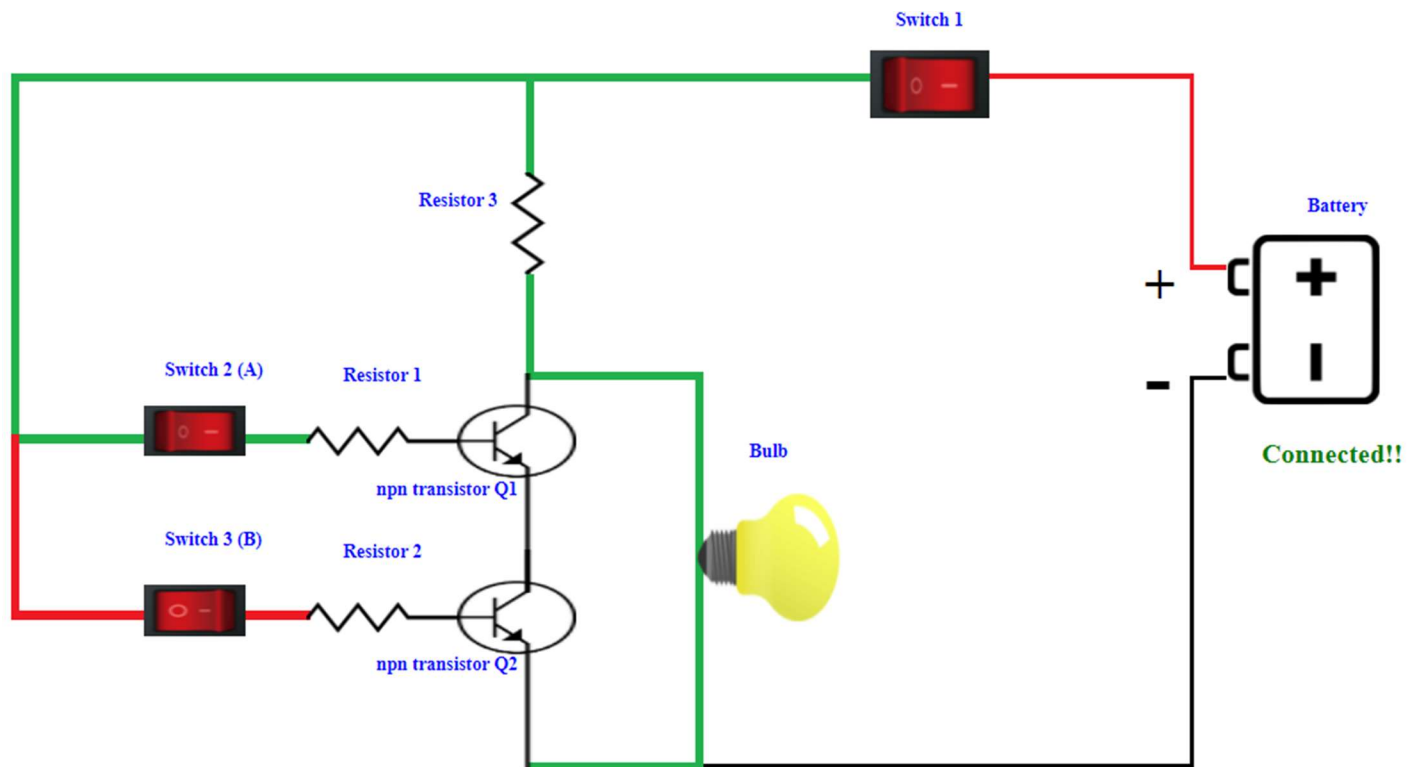


A = 1 and B = 0

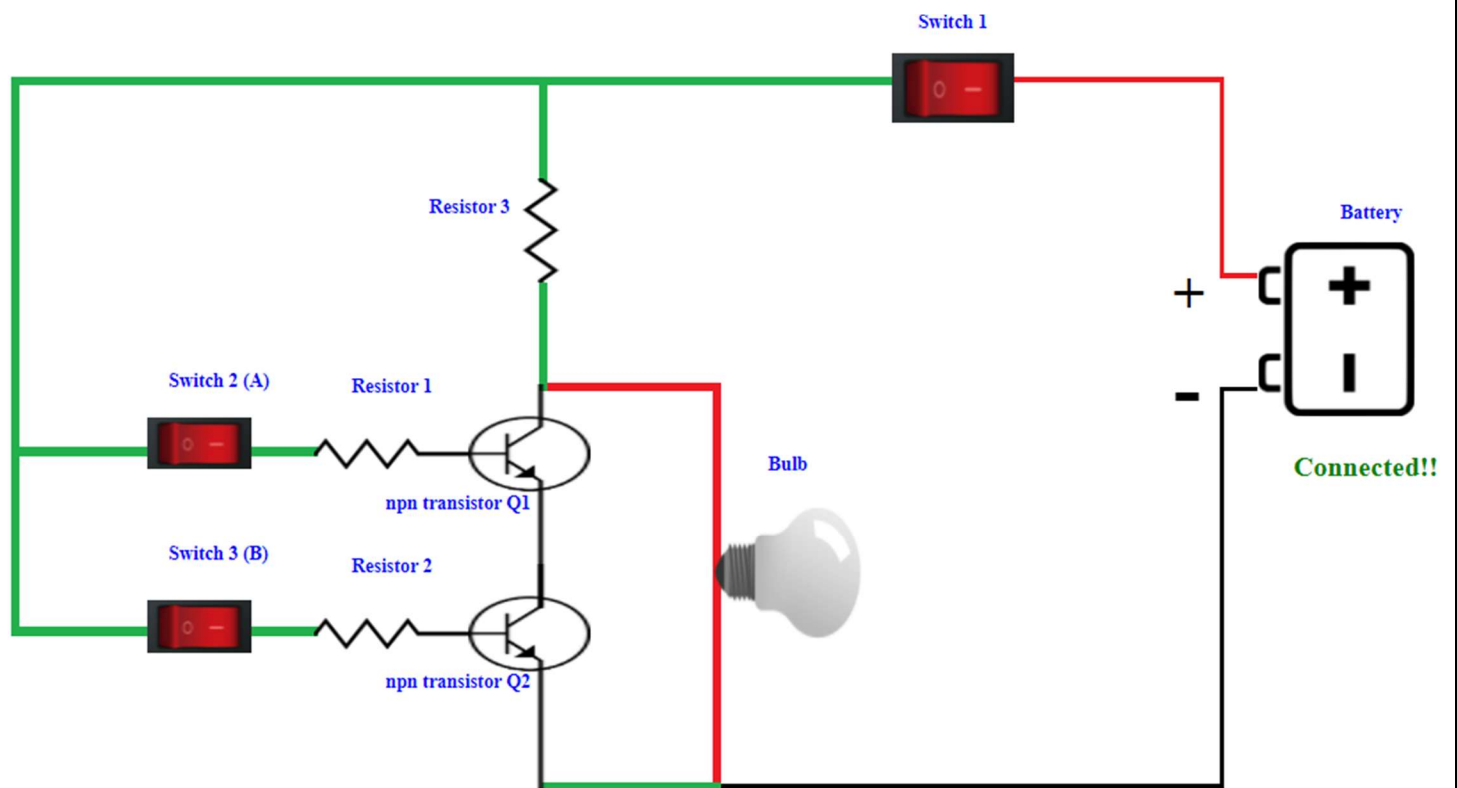

Both A and B are 1

NOR Gate


NOR gate is actually a series of OR gate with NOT gate. If we connect the output of an OR gate to the input of a NOT gate, this combination will work as NOT-OR or NOR gate. Its output is 0 when any or all inputs are 1, otherwise output is 1.

 


IC 7402

A	B	$Y = (A+B)'$
0	0	1
0	1	0
1	0	0
1	1	0



Truth table

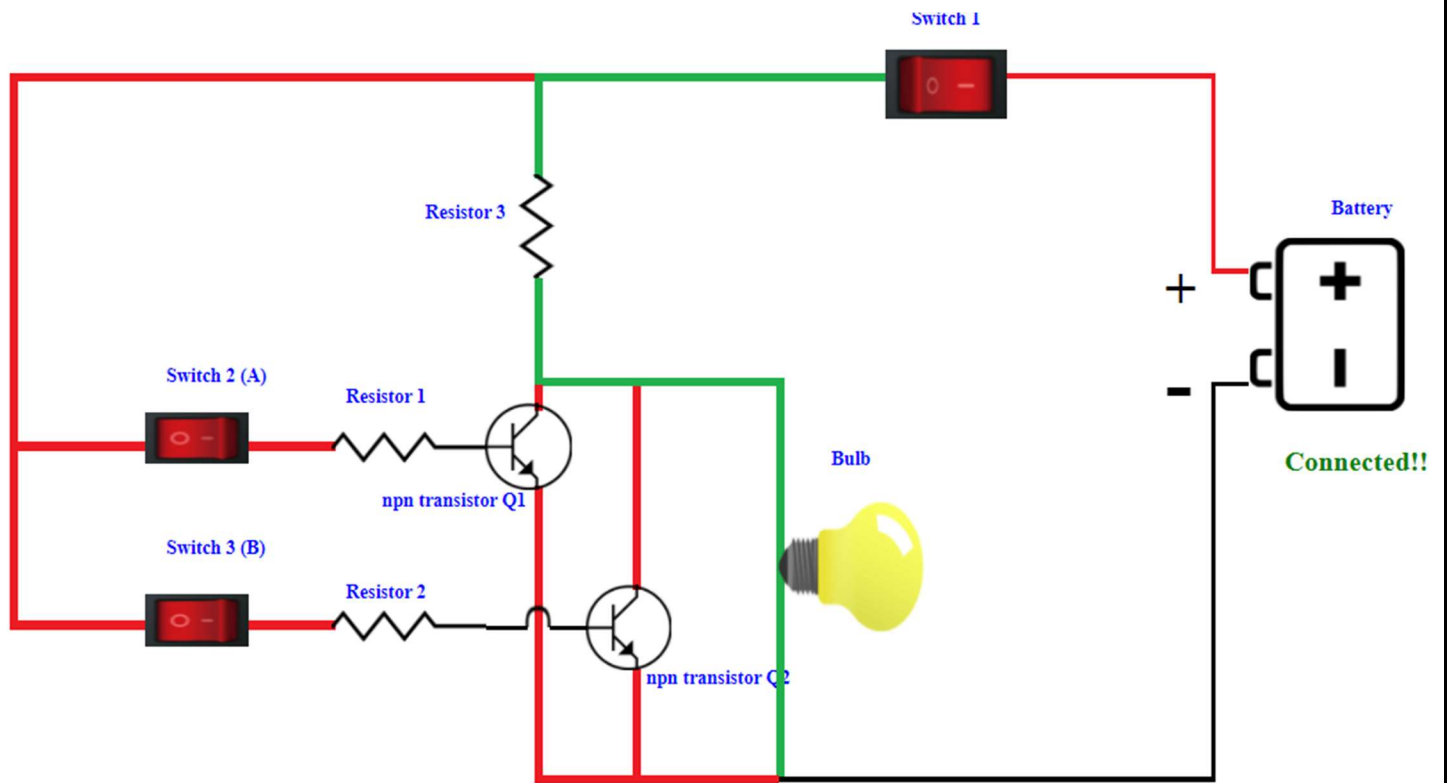

Both A and B are 0

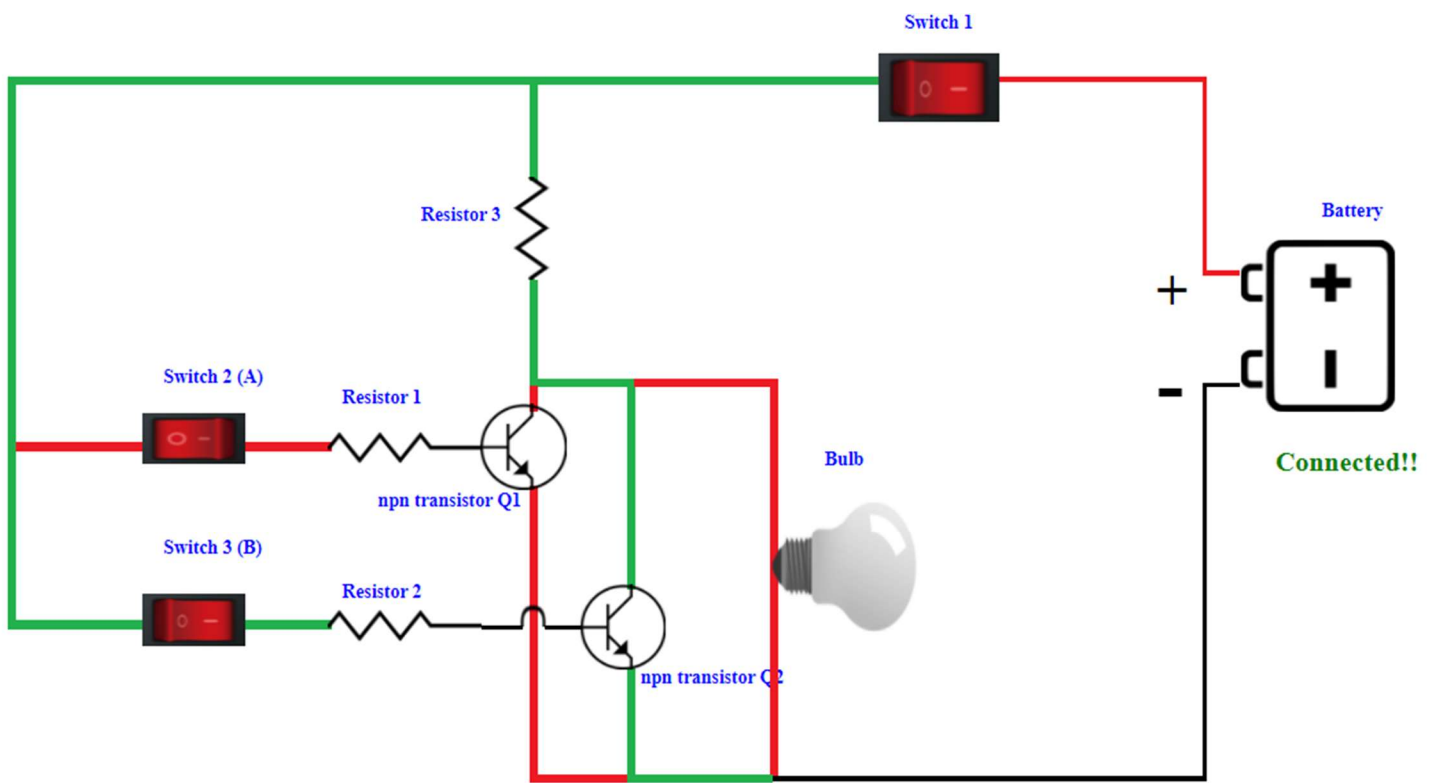


A = 0 and B = 1

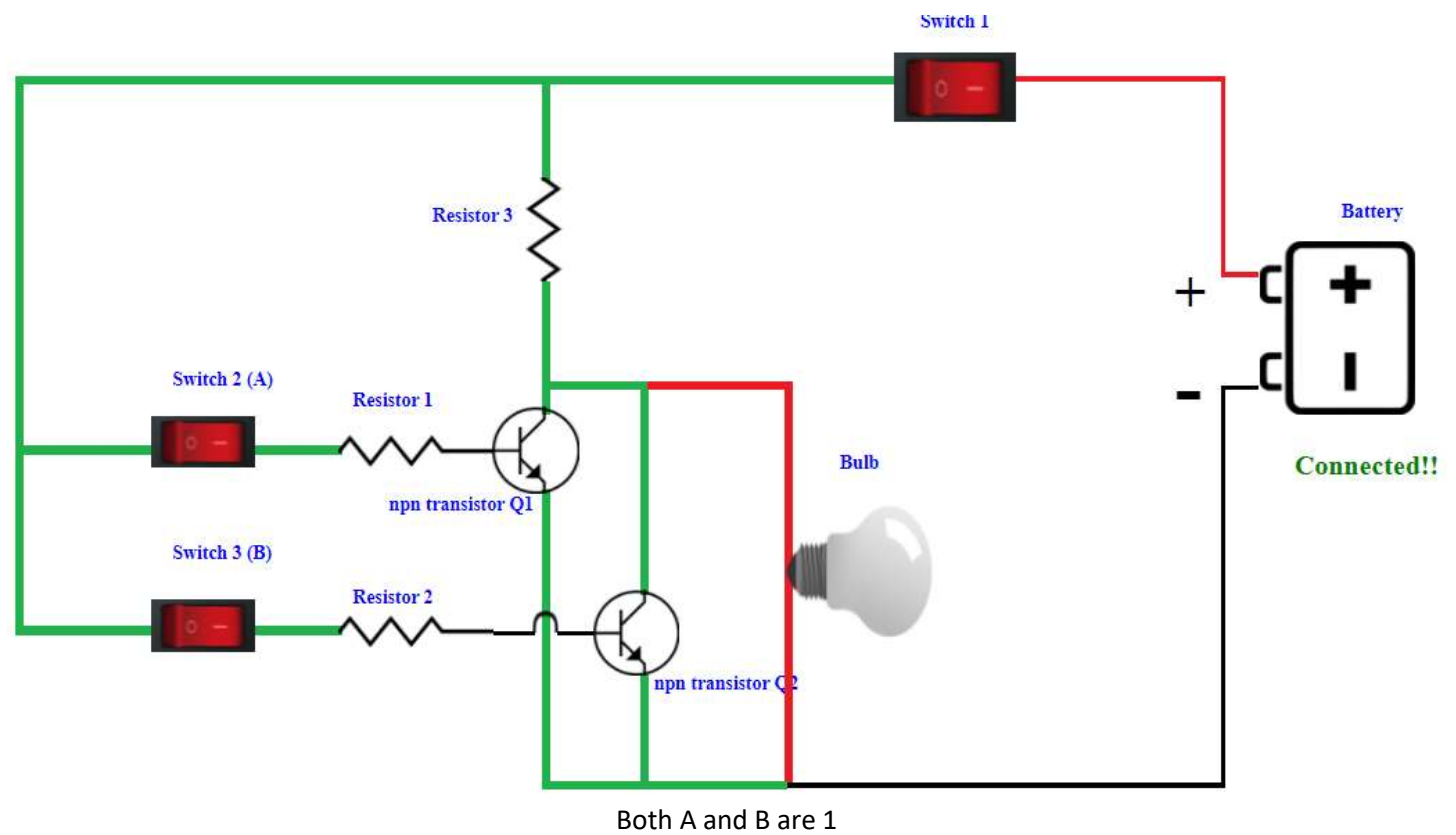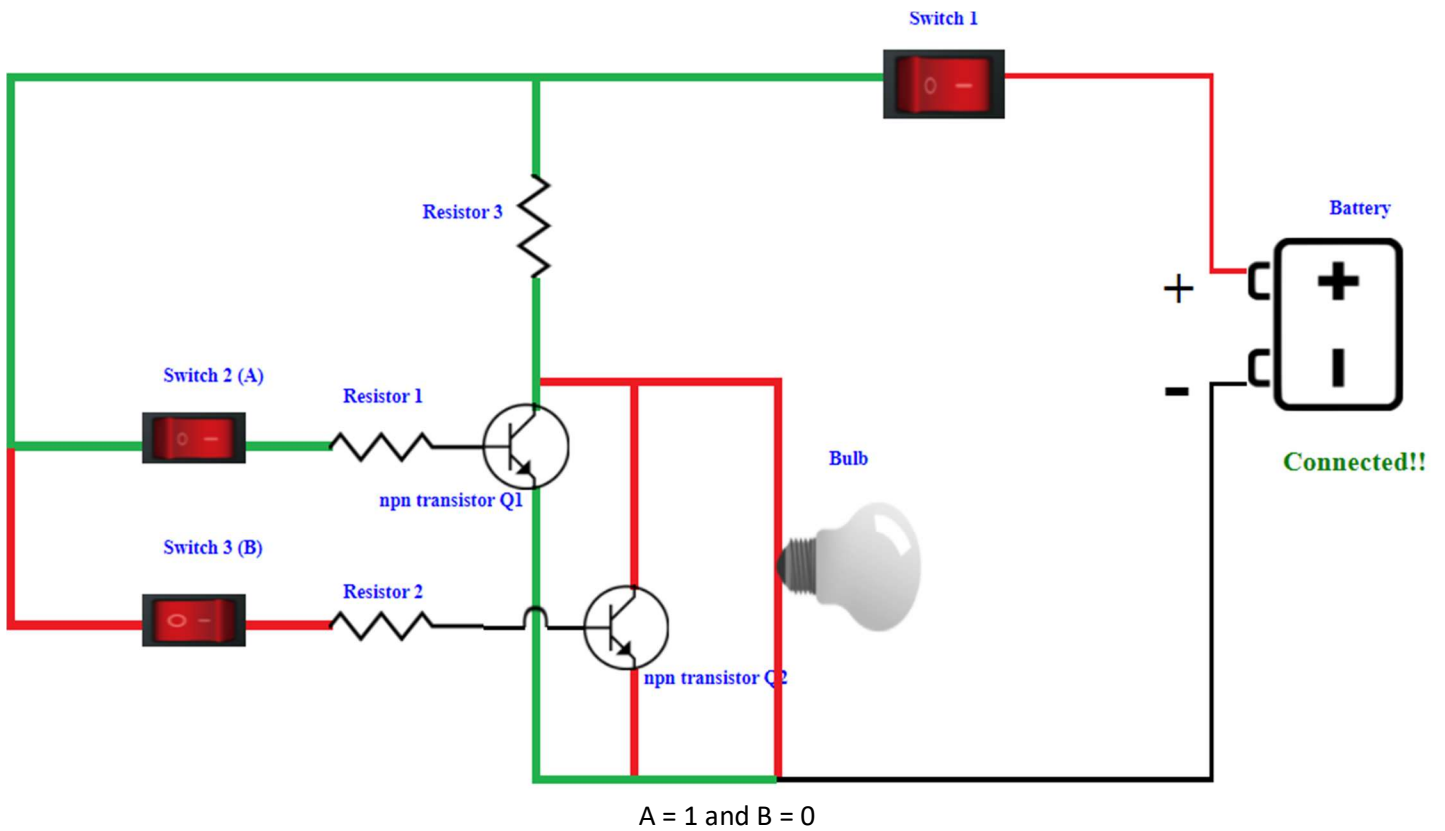

Exclusive OR (X-OR) Gate



X-OR gate produces an output as 1, when number of 1's at its inputs is odd, otherwise output is 0. It has two inputs and one output.

 


IC 7486


A	B	Y = A XOR B
0	0	0
0	1	1
1	0	1
1	1	0

Truth table

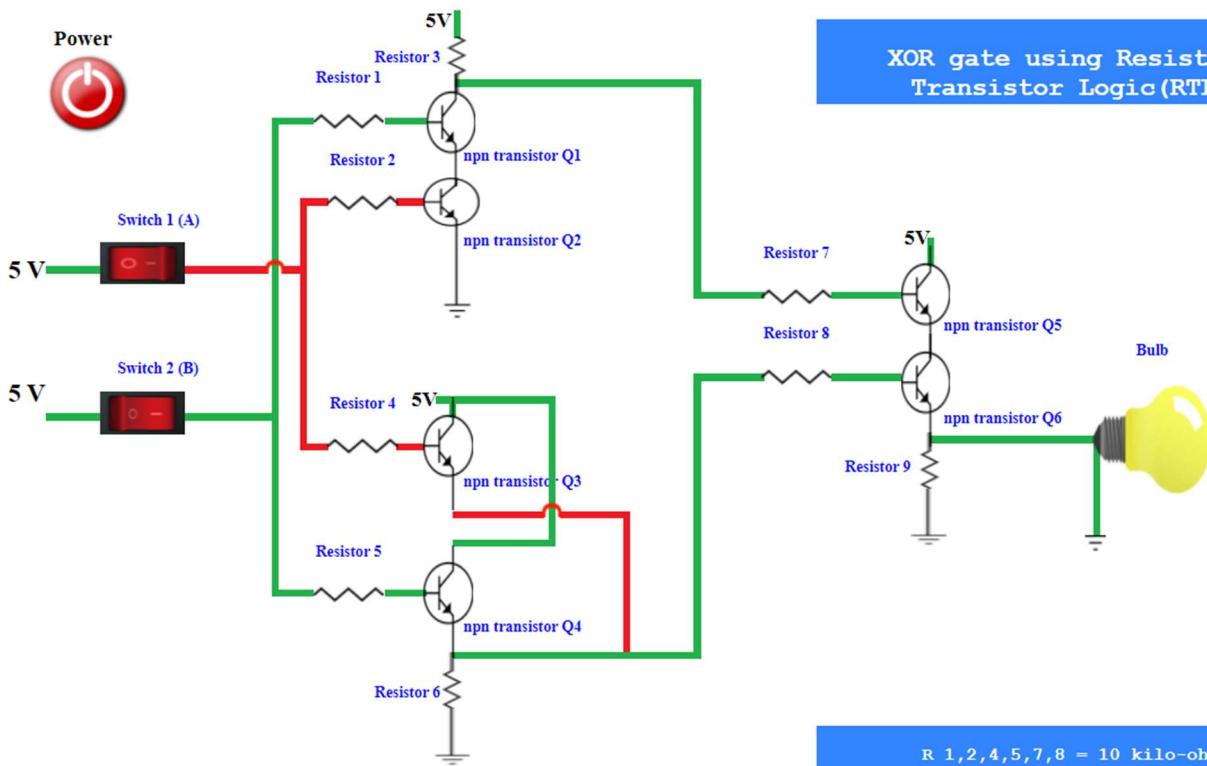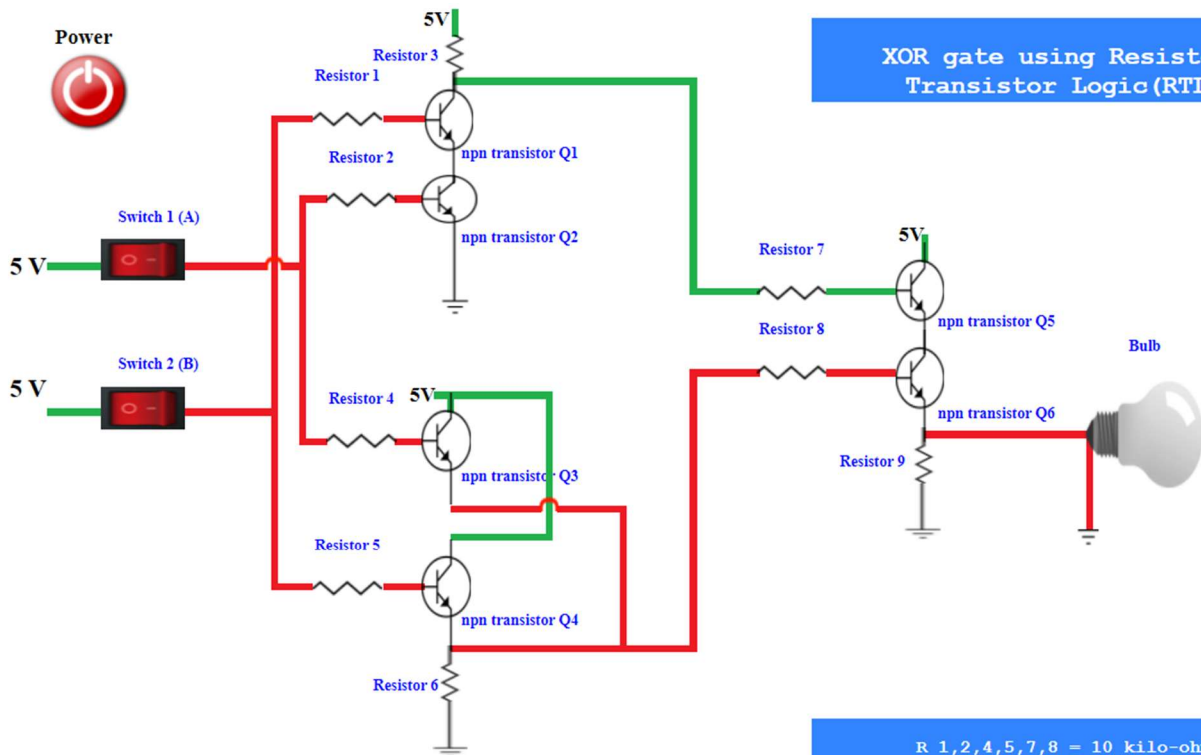

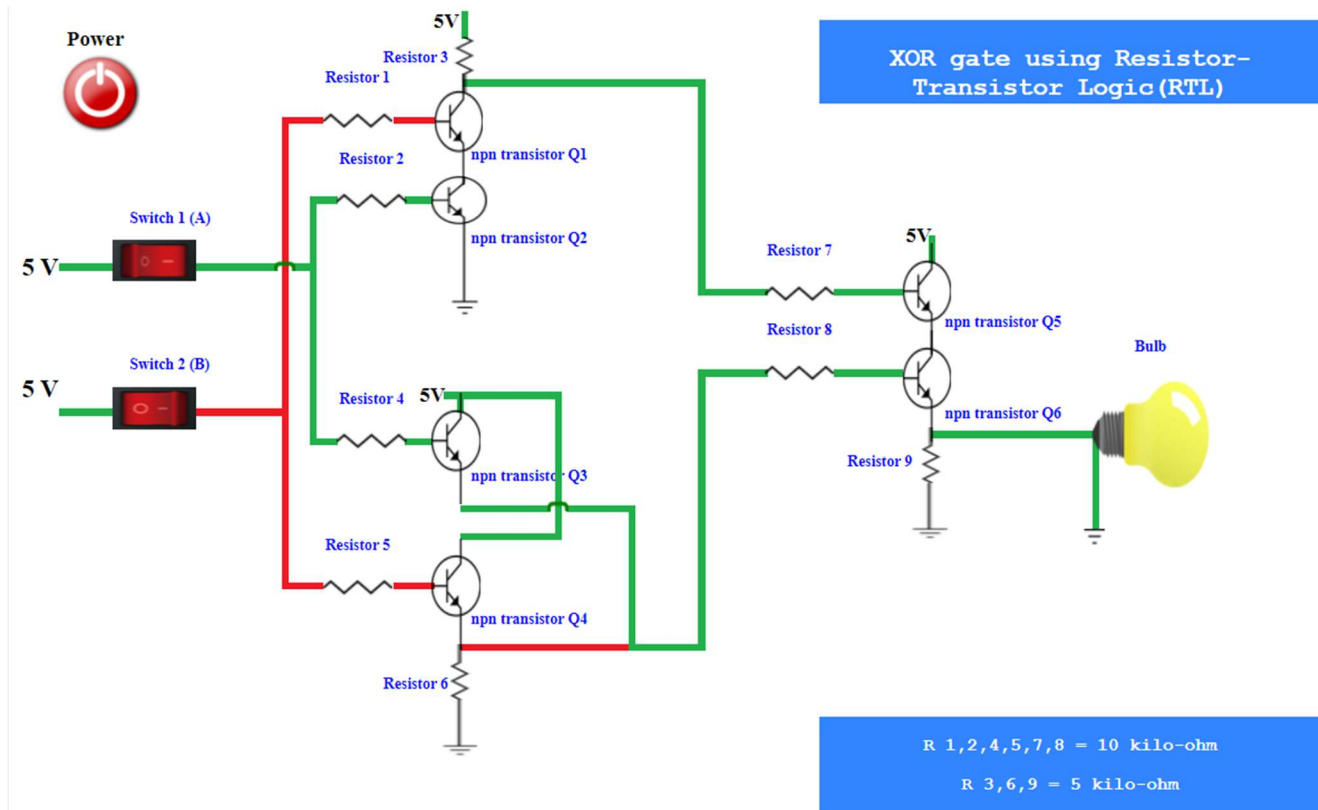


A = 1 and B = 0

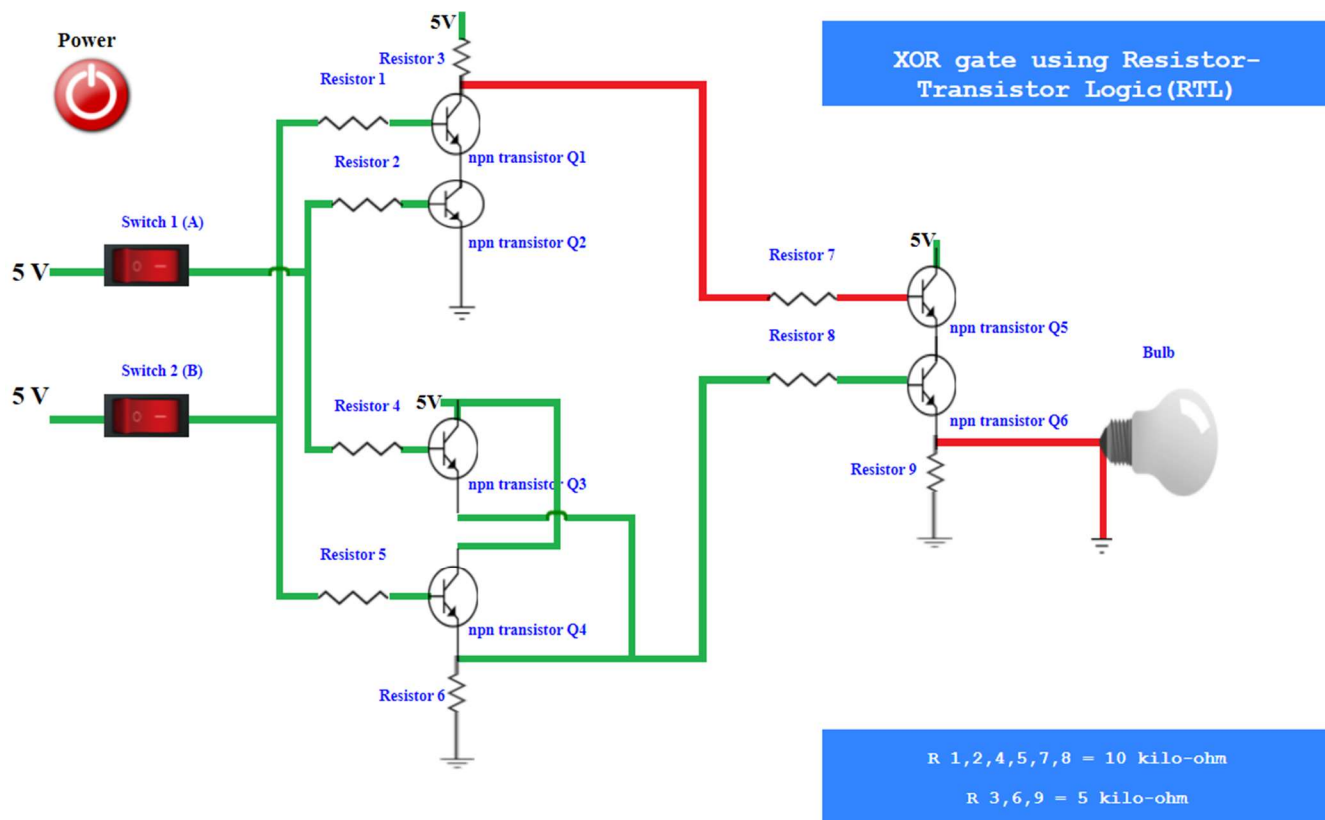

Both A and B are 1

Exclusive NOR (X-NOR) Gate

 X-NOR gate produces an output as 1, when number of 1's at its inputs is not odd, otherwise output is 0. It has two inputs and one output.



A	B	Y = A XNOR B
0	0	1
0	1	0
1	0	0
1	1	1

Truth table

